

Answer 1

A	B	Q
1	1	0
1	0	1
0	1	1
0	0	0

AO1.2

2

1 mark for the first two rows

1 mark for the last two rows

Answer 2

A	B	C _{in}	S	C _{out}
1	1	1	1	1
1	1	0	0	1
1	0	1	0	1
1	0	0	1	0
0	1	1	0	1
0	1	0	1	0
0	0	1	1	0
0	0	0	0	0

1 Mark for rows 1 and 2

1 Mark for rows 3 and 4

1 Mark for rows 5 and 6

1 Mark for rows 7 and 8

Answer 3

- Circuit adds two bits (and a carry bit) together/is an adder.
 - A B and C_{in} are added together
 - The result is given in S
 - And a carry bit in C_{out}
- (1 per -)

AO2.2

4